

## Computers Logic and CPU

Patrice Koehl  
Computer Science  
UC Davis



## Computers

Logic: acting on information

The Central Processing Unit (CPU)

Elements of a Computer

## Computers


Logic: acting on information

### The concept of pressure




When we remove the block, what is the effect on pressure?

### The concept of pressure

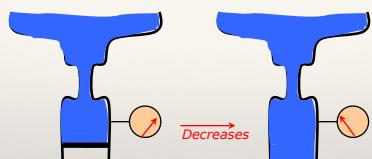

When we remove the block, what is the effect on pressure?

### Electrical pressure: voltage

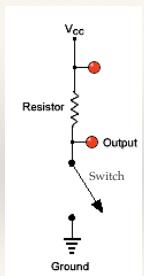

If switch is off (0) (equivalent to the presence of the block)

$V_{output} = V_{cc}$  high (i.e. 1)


If switch is on (1) (equivalent to the absence of the block)

$V_{output} < V_{cc}$  low (i.e. 0)

"Inverter"

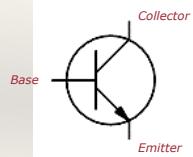
## The transistor

A transistor can be used as an electronic switch:





-if  $V_{base}$  is high, the current "flows" between the emitter and the collector (switch is on)

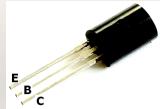-If  $V_{base}$  is low, the current does not pass (switch is off)






## The not gate

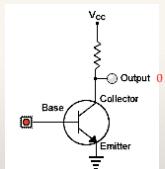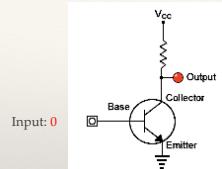


Input	Output
0	1
1	0

## The not-and (NAND) gate

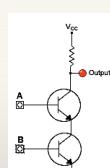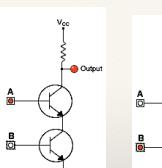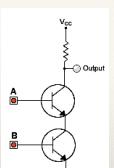


Input A	Input B	Output
1	1	0
1	0	1
0	1	1
0	0	1


The AND gate

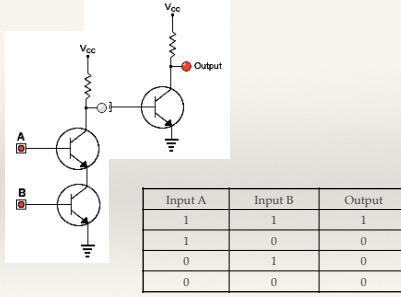

The not-or (NOR) gate

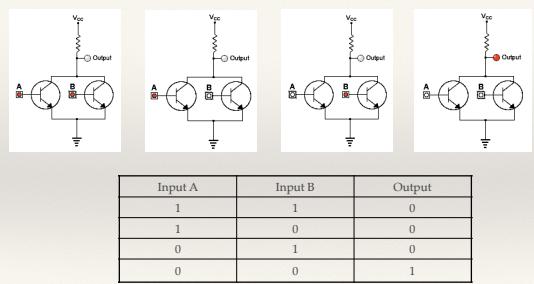

The OR gate

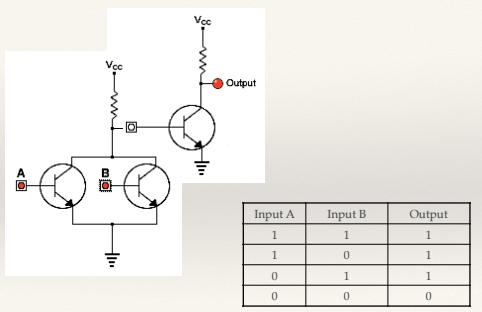


Type	Distinctive shape	Rectangular shape	Boolean logic between A & B	Truth table												
AND			$A \cdot B$	<table border="1"> <thead> <tr> <th>INPUT</th> <th>OUTPUT</th> </tr> </thead> <tbody> <tr> <td>A: 0</td> <td>0: 0</td> </tr> <tr> <td>0: 0</td> <td>0: 0</td> </tr> <tr> <td>0: 1</td> <td>0: 0</td> </tr> <tr> <td>1: 0</td> <td>0: 0</td> </tr> <tr> <td>1: 1</td> <td>1: 1</td> </tr> </tbody> </table>	INPUT	OUTPUT	A: 0	0: 0	0: 0	0: 0	0: 1	0: 0	1: 0	0: 0	1: 1	1: 1
INPUT	OUTPUT															
A: 0	0: 0															
0: 0	0: 0															
0: 1	0: 0															
1: 0	0: 0															
1: 1	1: 1															
OR			$A + B$	<table border="1"> <thead> <tr> <th>INPUT</th> <th>OUTPUT</th> </tr> </thead> <tbody> <tr> <td>A: 0</td> <td>0: 0</td> </tr> <tr> <td>0: 0</td> <td>0: 0</td> </tr> <tr> <td>0: 1</td> <td>0: 1</td> </tr> <tr> <td>1: 0</td> <td>1: 1</td> </tr> <tr> <td>1: 1</td> <td>1: 1</td> </tr> </tbody> </table>	INPUT	OUTPUT	A: 0	0: 0	0: 0	0: 0	0: 1	0: 1	1: 0	1: 1	1: 1	1: 1
INPUT	OUTPUT															
A: 0	0: 0															
0: 0	0: 0															
0: 1	0: 1															
1: 0	1: 1															
1: 1	1: 1															
NOT			$\bar{A}$	<table border="1"> <thead> <tr> <th>INPUT</th> <th>OUTPUT</th> </tr> </thead> <tbody> <tr> <td>A: 0</td> <td>0: 1</td> </tr> <tr> <td>0: 1</td> <td>0: 0</td> </tr> </tbody> </table>	INPUT	OUTPUT	A: 0	0: 1	0: 1	0: 0						
INPUT	OUTPUT															
A: 0	0: 1															
0: 1	0: 0															
NAND			$\bar{A} \cdot \bar{B}$	<table border="1"> <thead> <tr> <th>INPUT</th> <th>OUTPUT</th> </tr> </thead> <tbody> <tr> <td>A: 0</td> <td>0: 1</td> </tr> <tr> <td>0: 0</td> <td>1: 1</td> </tr> <tr> <td>0: 1</td> <td>0: 1</td> </tr> <tr> <td>1: 0</td> <td>0: 1</td> </tr> <tr> <td>1: 1</td> <td>0: 0</td> </tr> </tbody> </table>	INPUT	OUTPUT	A: 0	0: 1	0: 0	1: 1	0: 1	0: 1	1: 0	0: 1	1: 1	0: 0
INPUT	OUTPUT															
A: 0	0: 1															
0: 0	1: 1															
0: 1	0: 1															
1: 0	0: 1															
1: 1	0: 0															
NOR			$\bar{A} + \bar{B}$	<table border="1"> <thead> <tr> <th>INPUT</th> <th>OUTPUT</th> </tr> </thead> <tbody> <tr> <td>A: 0</td> <td>0: 1</td> </tr> <tr> <td>0: 0</td> <td>1: 1</td> </tr> <tr> <td>0: 1</td> <td>0: 1</td> </tr> <tr> <td>1: 0</td> <td>0: 1</td> </tr> <tr> <td>1: 1</td> <td>0: 0</td> </tr> </tbody> </table>	INPUT	OUTPUT	A: 0	0: 1	0: 0	1: 1	0: 1	0: 1	1: 0	0: 1	1: 1	0: 0
INPUT	OUTPUT															
A: 0	0: 1															
0: 0	1: 1															
0: 1	0: 1															
1: 0	0: 1															
1: 1	0: 0															

[http://en.wikipedia.org/w/index.php?title=Logic\\_gate](http://en.wikipedia.org/w/index.php?title=Logic_gate)


## Computers

The Central Processing Unit (CPU)

CPU

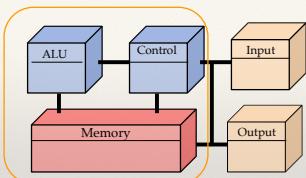

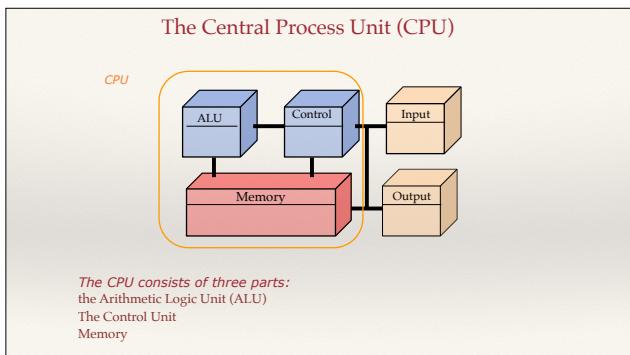The CPU consists of three parts:  
the Arithmetic Logic Unit (ALU)  
The Control Unit  
Memory




## The Fetch/Execute Cycle

The CPU cycles through a series of operations or instructions, organized in a cycle, the Fetch/Execute cycle:

1. Instruction Fetch (IF)
2. Instruction Decode (DP)
3. Data Fetch (DF)
4. Instruction Execute (IE)
5. Result Return


### Step 1: Instruction Fetch

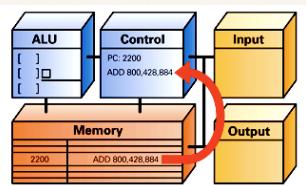

Fetch instruction from memory position 2200:

Add numbers in memory positions 884 and 428, and store results at position 800


### Step 2: Instruction Decode

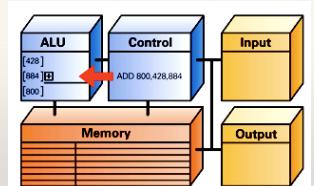

Decode instruction:

Defines operation (+), and set memory pointers in ALU


### Step 3: Data Fetch

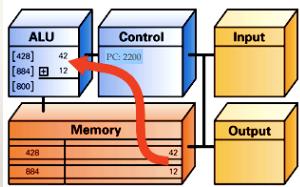

Fetch data:

Get numbers at memory positions 428 and 884: 42 and 12  
and put in ALU


### Step 4: Instruction Execution

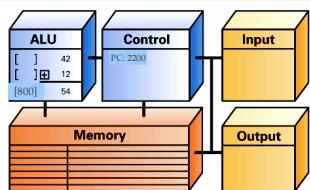

Execute:

Add numbers 42 and 12 in ALU: 54

### Step 5: Return Result

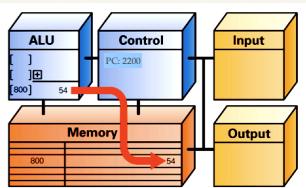

Return:

Put results (54) in position 800 in memory

## Possible operations

Computers can only perform about 100 different types of operations; all other operations must be broken down into simpler operations among these 100.

*Some of these operations:*


- Add, Mult, Div
- AND, OR, NAND, NOR, ...
- Bit shifts
- Test if a bit is 0 or 1
- Move information in memory
- ...




## Repeating the F/E cycle

Computers get their impressive capabilities by performing many of these F/E cycles per second.

The **computer clock** determines the rate of F/E cycles per second; it is now expressed in GHz, i.e. in billions of cycles per seconds!

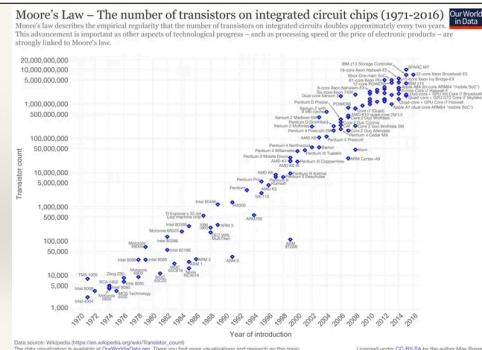*Note that the rate given is not an exact measurement.*




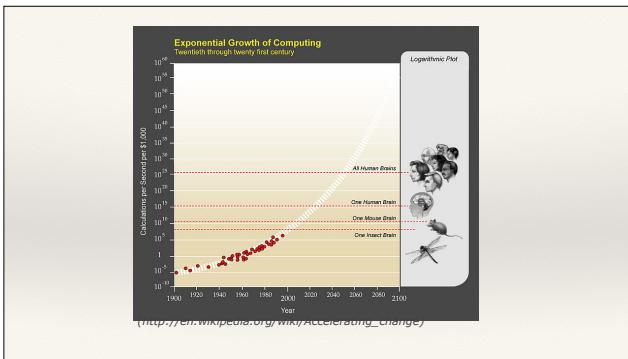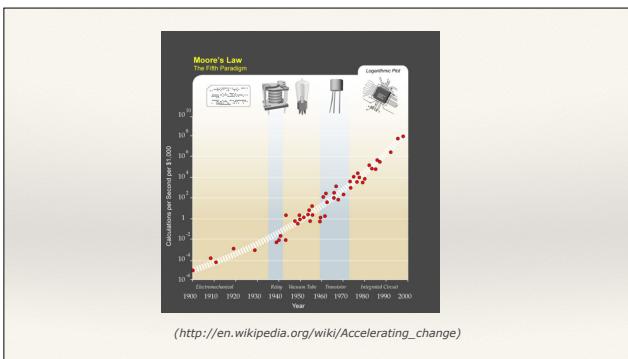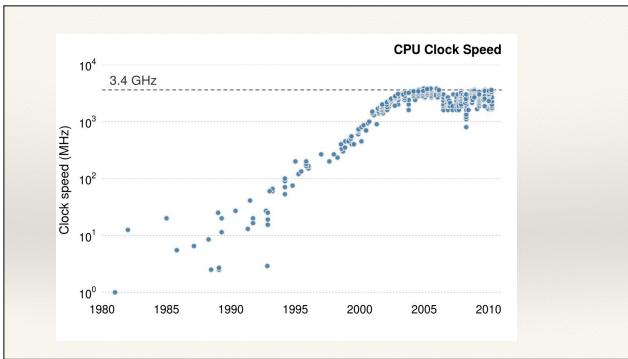

## Computers

Elements of a Computer

### Computer: basic scheme

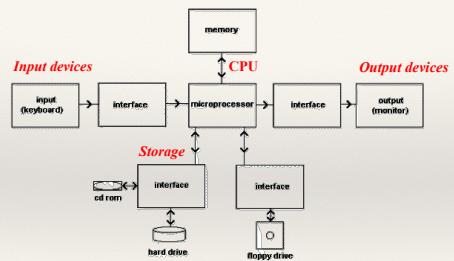

### The Central Process Unit (CPU)



CPU's are getting smaller, and can include more than one "core" (or processors).



CPU's get hot, as their internal components dissipate heat: it is important to add a heat sink and fans to keep them cool.

