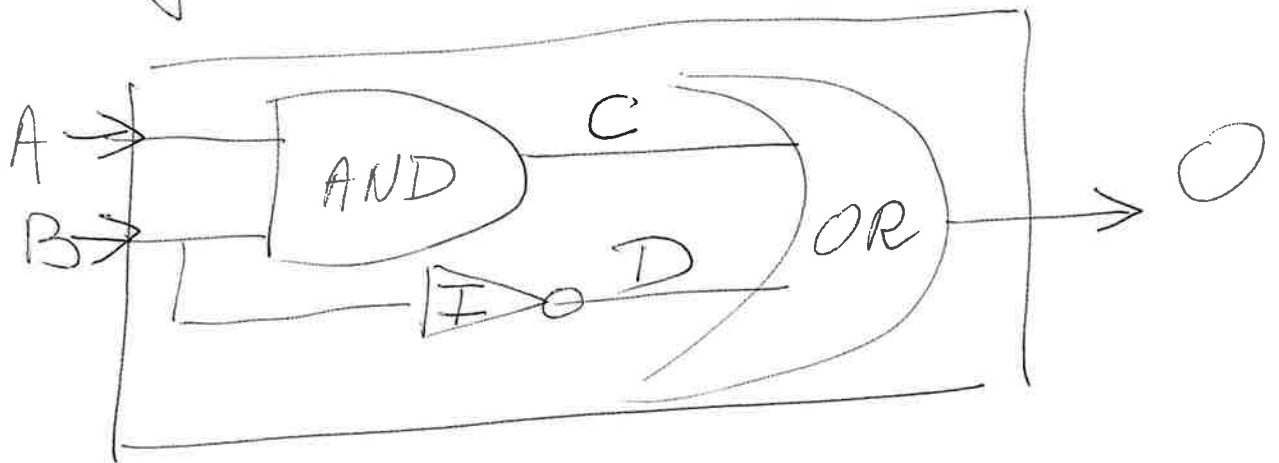


Discussion 1/26/26

①

Exercise 1

Characterize the circuit:



Logic table:

A	B	C	D	O
1	1	1	0	1
1	0	0	1	1
0	1	0	0	0
0	0	0	1	1

$$\begin{aligned} O &= C + D \\ &= A \cdot B + \overline{B} \end{aligned}$$

Exercise 2:


(2)

Build the diagram and logic table for the Boolean expression

$$O = A \cdot \bar{B} + \bar{A} \cdot B$$

Can you simplify it?

Step : build the circuit.

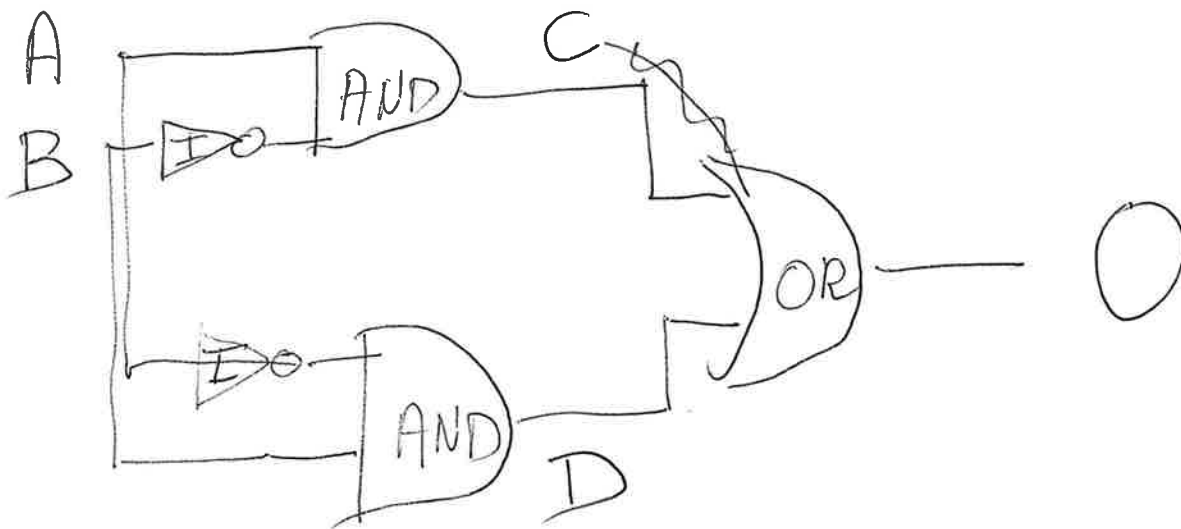

A	B	$\bar{A}$	$\bar{B}$	C	D	O
1	1	0	0	0	0	0
1	0	0	1	1	0	1
0	1	1	0	0	1	1
0	0	1	1	0	0	0

(3)

Therefore:


$$A \oplus B = A \bar{B} + \bar{A} B$$

$$\overline{A \oplus B} = \overline{A \bar{B} + \bar{A} B}$$

$$= \overline{A \bar{B}} \cdot \overline{\bar{A} B}$$

$$= (\bar{A} + B) \cdot (A + \bar{B})$$


$$= (\bar{A} + B) \cdot (A + \bar{B})$$

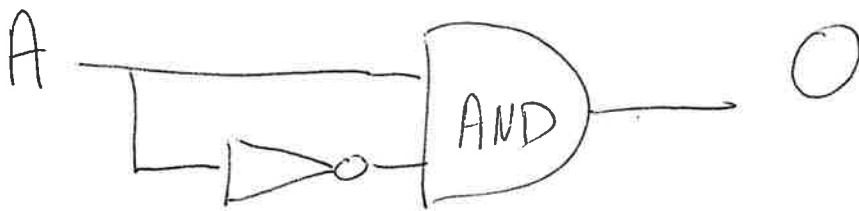Exercise 3:

A	$\bar{A}$	O
1	0	0
0	1	0

Building a circuit with logic gate: ④

A	B	O
1	1	1
1	0	0
0	1	1
0	0	0

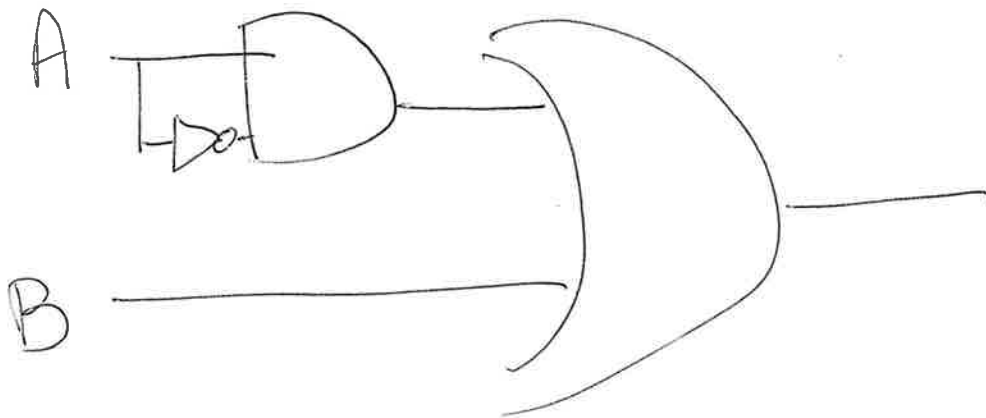

You are on the island of knights ^(S)
and knaves. You meet John,
Kai, and Tania.


John: Tania is not a knave

Kai: John and Tania are knights

Tania: John is a knight or Kai is
a knave (inclusive).

Step 1: (K: knight, N: knave)

John	Kai	Tania	S ₁	S ₂	S ₃	
K	K	K	T	T	T	
<u>(K)</u>	K	N	<u>(F)</u>	F	T	X
K	<u>(N)</u>	K	T	<u>(T)</u>	T	X
<u>(K)</u>	N	N	<u>(F)</u>	F	T	X
<u>(N)</u>	K	K	<u>(T)</u>	F	F	X
N	<u>(K)</u>	N	F	<u>(F)</u>	F	X
<u>(N)</u>	N	K	<u>(T)</u>	F	T	X
N	N	<u>(N)</u>	F	F	<u>(T)</u>	X

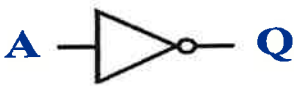NOT		$\bar{A}$ or $\neg A$	<table><tr><th>Input</th><th>Output</th></tr><tr><td>A</td><td>Q</td></tr><tr><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td></tr></table>	Input	Output	A	Q	1	0	0	1										
Input	Output																				
A	Q																				
1	0																				
0	1																				
OR		$A+B$ or $A \vee B$	<table><tr><th>Input 1</th><th>Input 2</th><th>Output</th></tr><tr><td>A</td><td>B</td><td>Q</td></tr><tr><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>0</td><td>0</td></tr></table>	Input 1	Input 2	Output	A	B	Q	1	1	1	1	0	1	0	1	1	0	0	0
Input 1	Input 2	Output																			
A	B	Q																			
1	1	1																			
1	0	1																			
0	1	1																			
0	0	0																			
AND		$A \cdot B$ or $A \wedge B$	<table><tr><th>Input 1</th><th>Input 2</th><th>Output</th></tr><tr><td>A</td><td>B</td><td>Q</td></tr><tr><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>0</td></tr></table>	Input 1	Input 2	Output	A	B	Q	1	1	1	1	0	0	0	1	0	0	0	0
Input 1	Input 2	Output																			
A	B	Q																			
1	1	1																			
1	0	0																			
0	1	0																			
0	0	0																			
XOR		$A \oplus B$	<table><tr><th>Input 1</th><th>Input 2</th><th>Output</th></tr><tr><td>A</td><td>B</td><td>Q</td></tr><tr><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>0</td><td>0</td></tr></table>	Input 1	Input 2	Output	A	B	Q	1	1	0	1	0	1	0	1	1	0	0	0
Input 1	Input 2	Output																			
A	B	Q																			
1	1	0																			
1	0	1																			
0	1	1																			
0	0	0																			
NOR		$\overline{A+B}$ or $\overline{A \vee B}$	<table><tr><th>Input 1</th><th>Input 2</th><th>Output</th></tr><tr><td>A</td><td>B</td><td>Q</td></tr><tr><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td></tr></table>	Input 1	Input 2	Output	A	B	Q	1	1	0	1	0	0	0	1	0	0	0	1
Input 1	Input 2	Output																			
A	B	Q																			
1	1	0																			
1	0	0																			
0	1	0																			
0	0	1																			
NAND		$\overline{A \cdot B}$ or $\overline{A \wedge B}$	<table><tr><th>Input 1</th><th>Input 2</th><th>Output</th></tr><tr><td>A</td><td>B</td><td>Q</td></tr><tr><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td></tr></table>	Input 1	Input 2	Output	A	B	Q	1	1	0	1	0	1	0	1	1	0	0	1
Input 1	Input 2	Output																			
A	B	Q																			
1	1	0																			
1	0	1																			
0	1	1																			
0	0	1																			
XNOR		$\overline{A \oplus B}$	<table><tr><th>Input 1</th><th>Input 2</th><th>Output</th></tr><tr><td>A</td><td>B</td><td>Q</td></tr><tr><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td></tr></table>	Input 1	Input 2	Output	A	B	Q	1	1	1	1	0	0	0	1	0	0	0	1
Input 1	Input 2	Output																			
A	B	Q																			
1	1	1																			
1	0	0																			
0	1	0																			
0	0	1																			