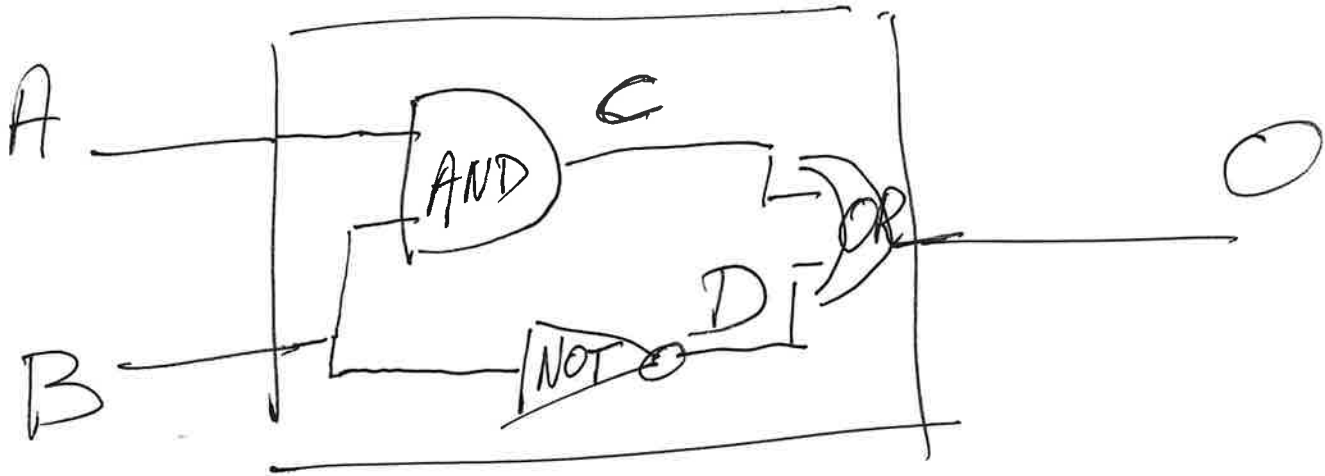


Exercise 1 :



Logic table

A	B	C	D	O
1	1	1	0	1
1	0	0	1	1
0	1	0	0	0
0	0	0	1	1

Boolean expression:

$$O = C + D$$

$$= A \cdot B + \overline{B}$$


Exercise 2

(2)

Build the diagram (circuit) and the logic table for the Boolean expression:

$$O = A \cdot \overline{B} + \overline{A} \cdot B$$

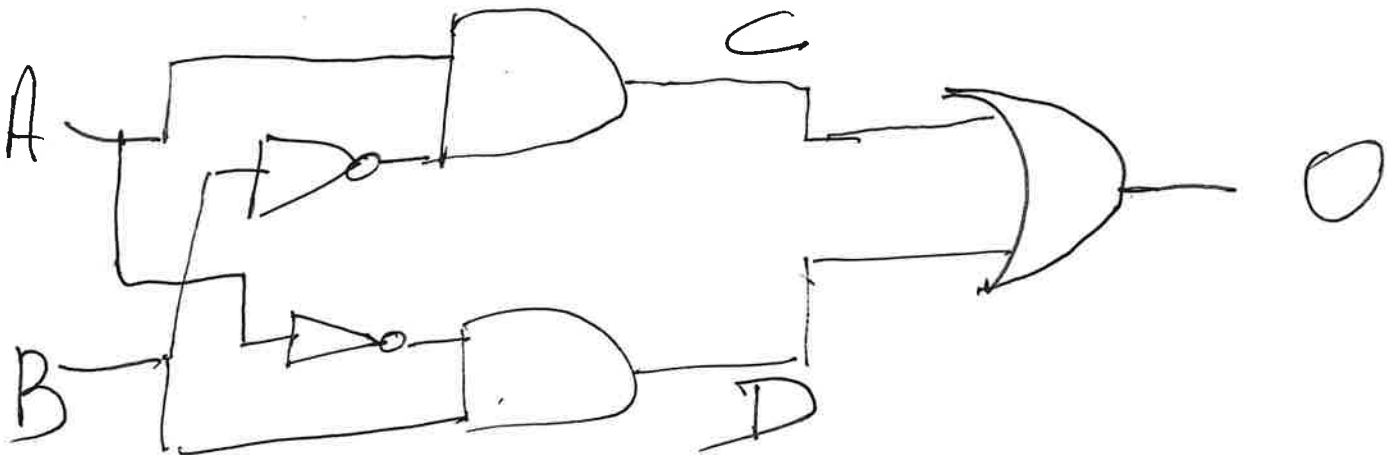$\downarrow \qquad \qquad \downarrow \qquad \qquad \downarrow$
AND OR AND



A	B	$\overline{A}$	$\overline{B}$	C	D	O
1	1	0	0	0	0	0
1	0	0	1	1	0	1
0	1	1	0	0	1	1
0	0	1	1	0	0	0

Therefore

$$A \bar{B} + \bar{A} B = A \oplus B$$

An interesting observation:

X NOR:

$$\overline{A \oplus B} = \overline{A \bar{B} + \bar{A} B}$$

$$= \overline{A \bar{B}} \cdot \overline{\bar{A} B}$$

$$= (\bar{A} + \bar{\bar{B}}) \cdot (\bar{\bar{A}} + \bar{B})$$

$$= (\bar{A} + B) \cdot (A + \bar{B})$$

Exercise 3

④



$$0 = A \cdot \overline{A}$$


logic table:

A	$\overline{A}$	0
1	0	0
0	1	0

Build a circuit with the logic table:

A	B	0
1	1	1
1	0	0
0	1	1
0	0	0

5

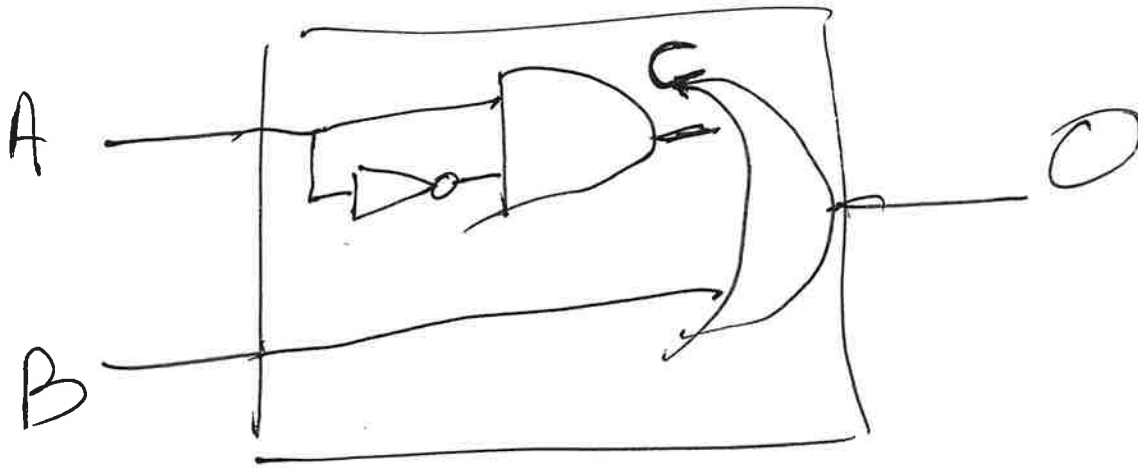

A	B	C	O
1	1	0	1
1	0	0	0
0	1	0	1
0	0	0	0

Exercise 4

To the island of knights and knaves.

You meet John, Kai, and Tania.

John: Tania is not a knave

Kai: John and Tania are knights


Tania: John is a knight or Kai is a knave
(inclusive).

K: knight; N: knave

	John	Kai	Tania	S_1	S_2	S_3
	K	K	K	T	T	F T
X	K	K	(N)	F	F	F T
X	K	(N)	K	T	(T)	F T
X	K	N	(N)	F	F	T T
X	(N)	K	K	(T)	F	F F
X	N	(K)	N	F	(F)	T F
X	(N)	N	K	(T)	F	F T
X	N	N	(N)	F	F	(T) T

All 3 are knights.

NOT

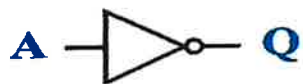

$\bar{A}$ or $\neg A$

Input	Output
A	Q
1	0
0	1

OR



$A+B$ or $A \vee B$

Input 1	Input 2	Output
A	B	Q
1	1	1
1	0	1
0	1	1
0	0	0


AND



$A \cdot B$ or $A \wedge B$

Input 1	Input 2	Output
A	B	Q
1	1	1
1	0	0
0	1	0
0	0	0

XOR

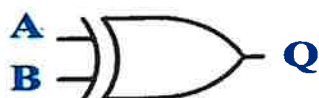

$A \oplus B$

Input 1	Input 2	Output
A	B	Q
1	1	0
1	0	1
0	1	1
0	0	0


NOR



$\overline{A+B}$ or $\overline{A \vee B}$

Input 1	Input 2	Output
A	B	Q
1	1	0
1	0	0
0	1	0
0	0	1

NAND

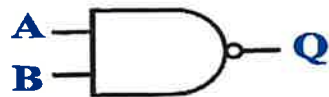

$\overline{A \cdot B}$ or $\overline{A \wedge B}$

Input 1	Input 2	Output
A	B	Q
1	1	0
1	0	1
0	1	1
0	0	1

XNOR



$\overline{A \oplus B}$

Input 1	Input 2	Output
A	B	Q
1	1	1
1	0	0
0	1	0
0	0	1