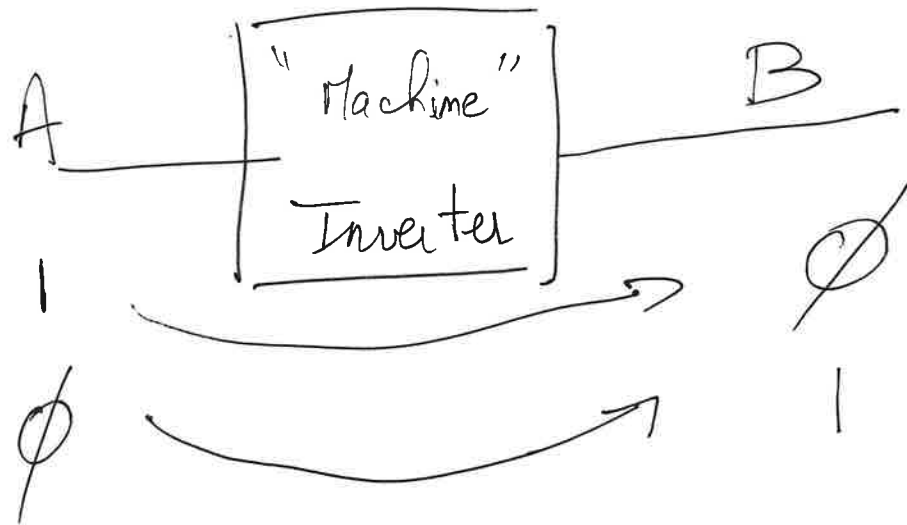



Compute

①


I) Simplest bit manipulation: Inverter



How could that work?

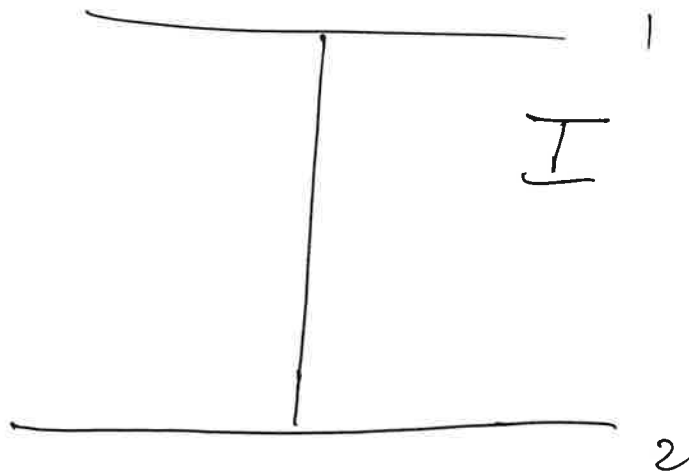



Controlled
by the
input

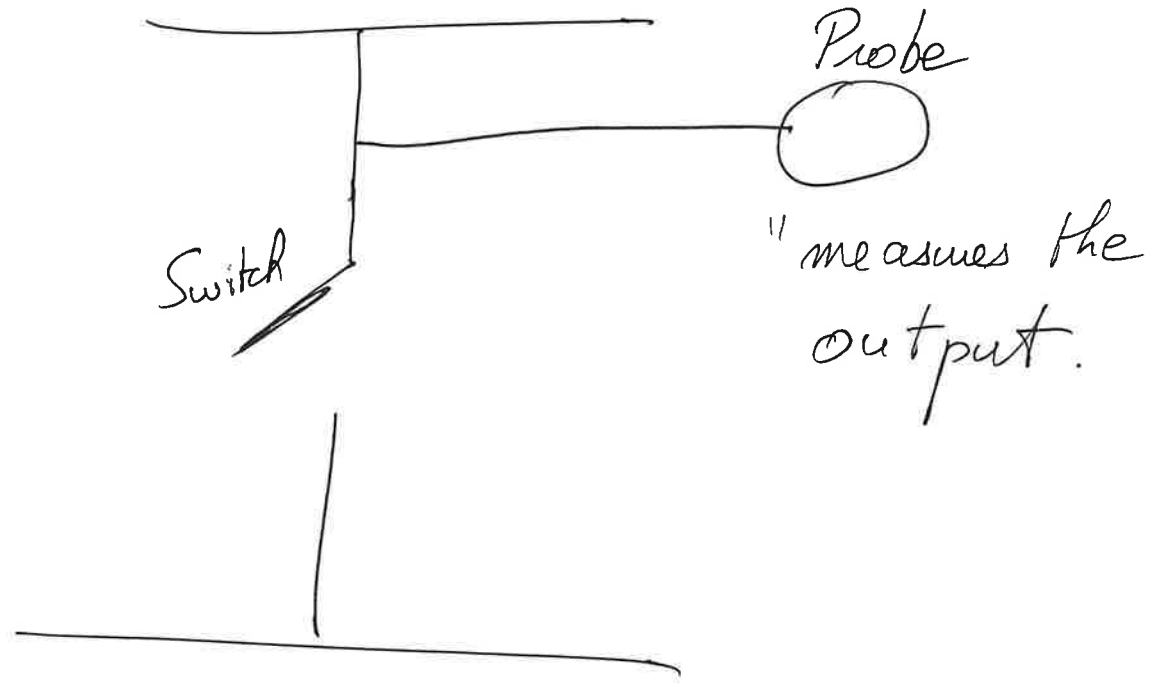


Probe: if the circuit is "working",
the probe does not detect anything
→ \emptyset

if the circuit is "broken",
then the probe reacts → 1

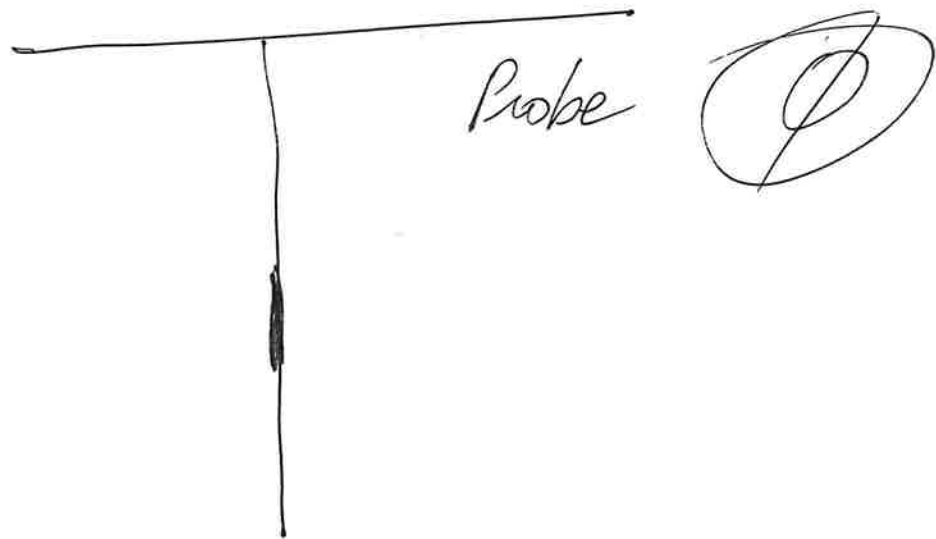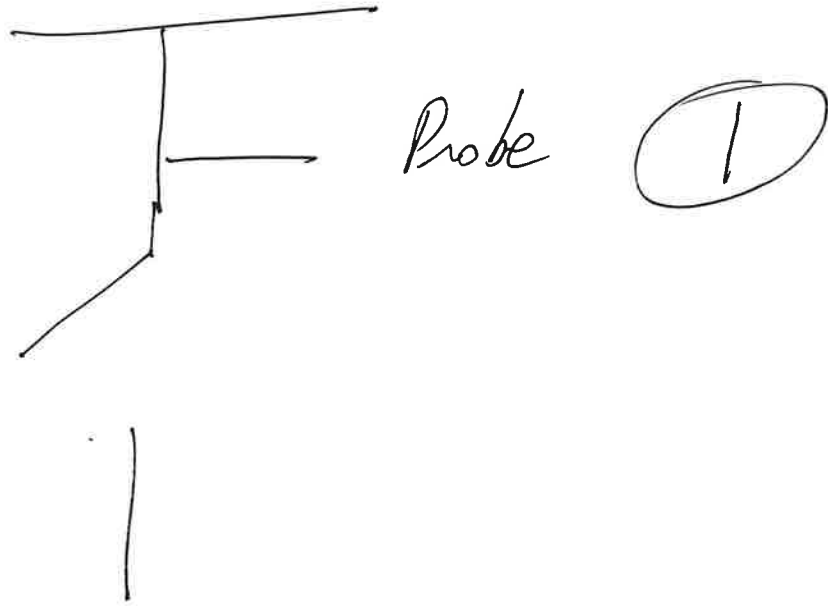Now let us see what happens
with switch / probe:




Represent it as Emitter

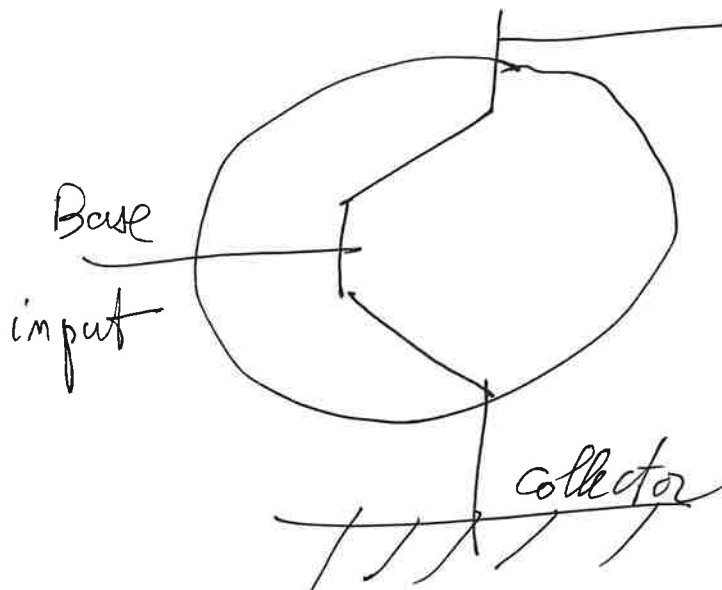


Output

transistors

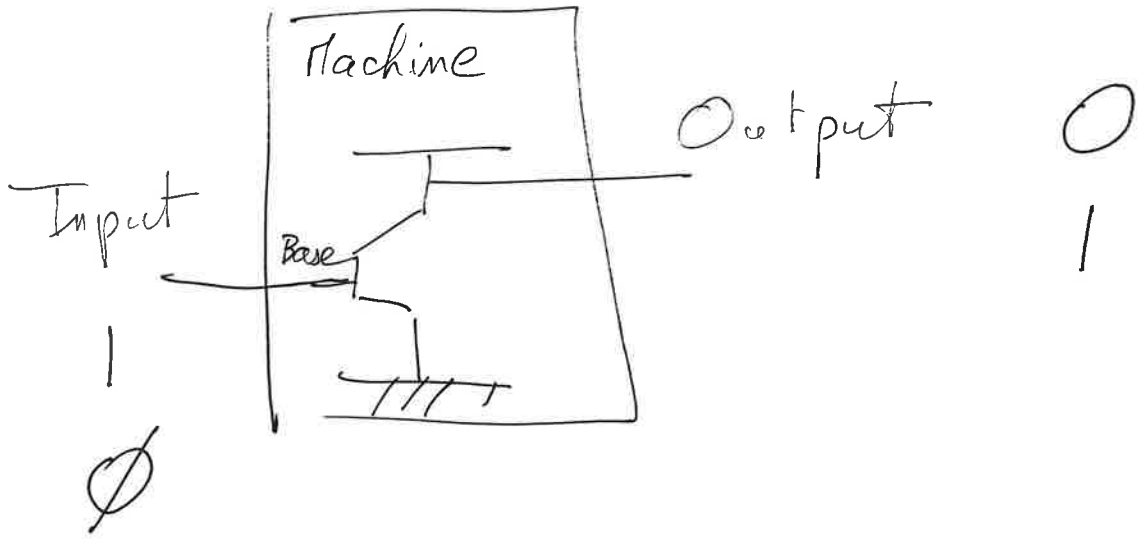


Inverter:

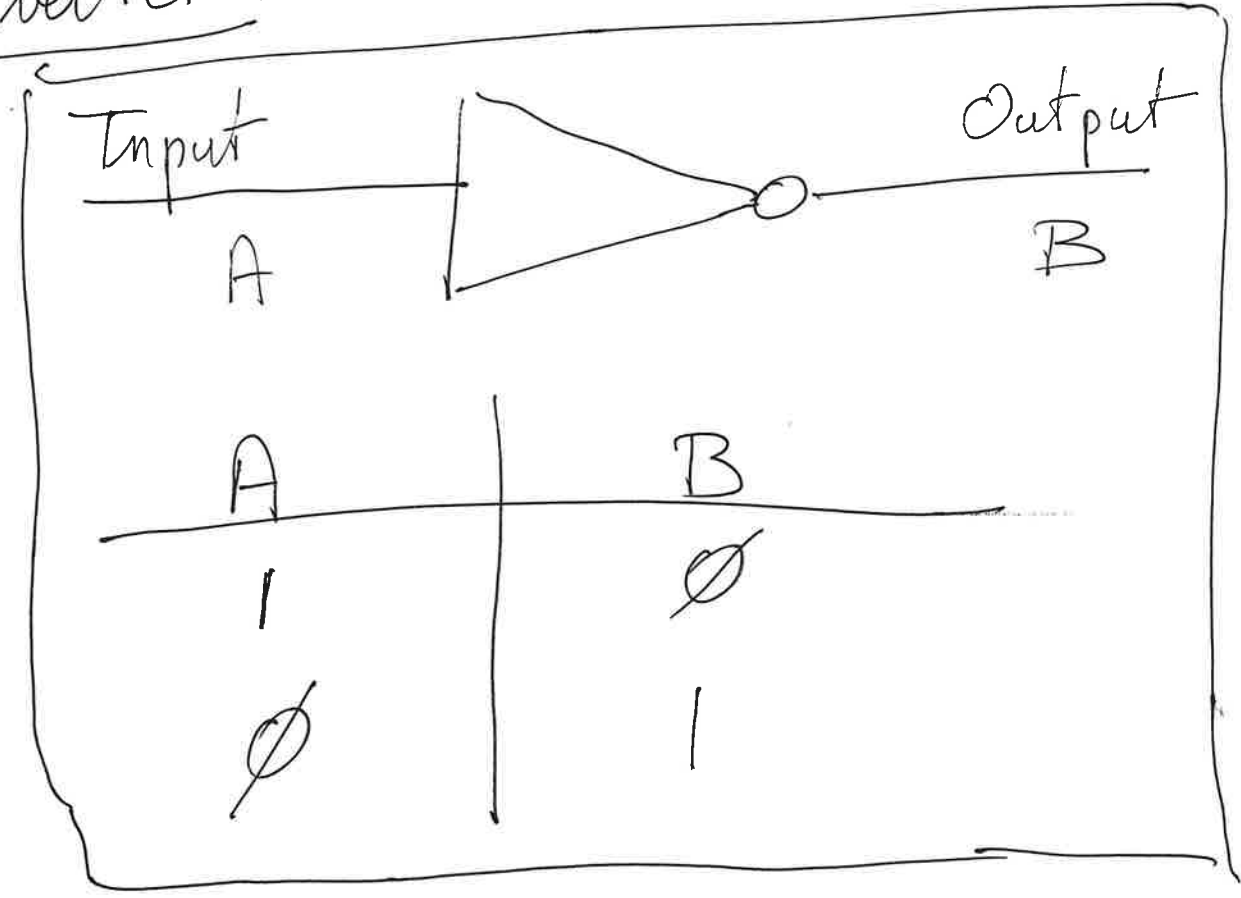


II) The multiplication

(5)

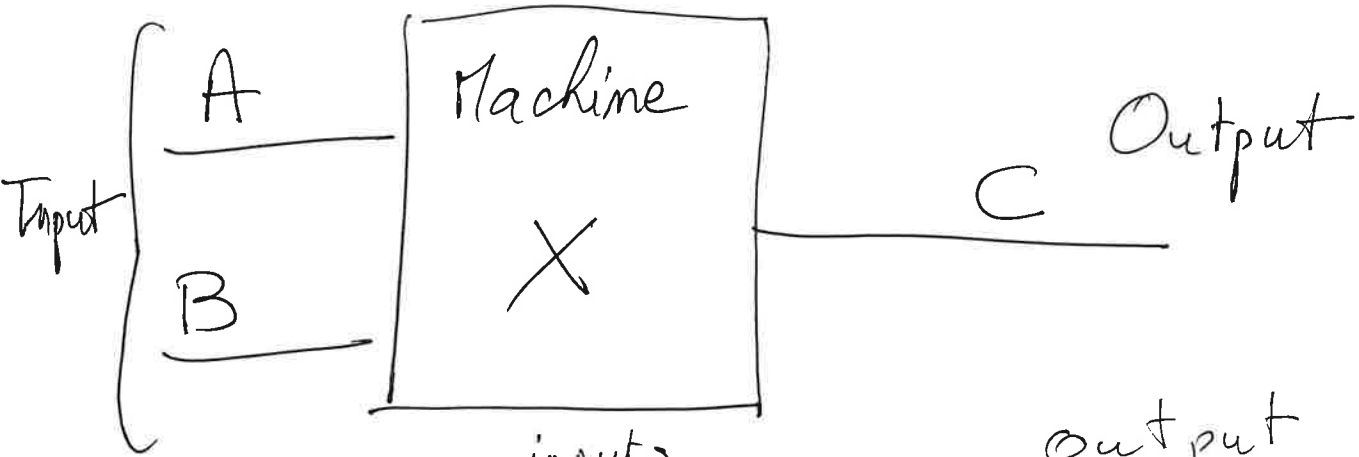

inputs		output
A	B	C
1	1	1
1	0	0
0	1	0
0	0	0

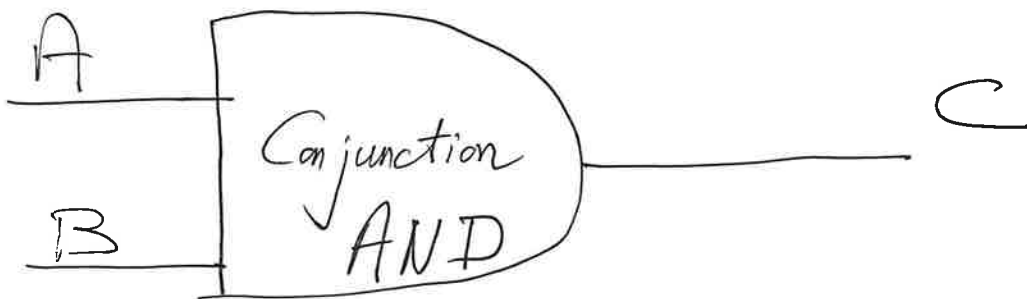

In math,

$$A \times B = C$$


In logic
√

$$A \cdot B = C$$

or

$$A \wedge B = C$$

Combining machines:

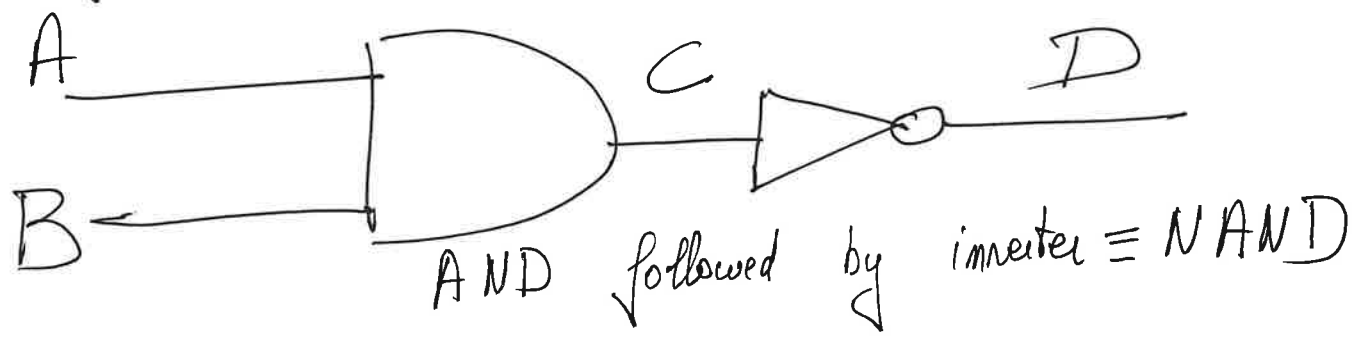

A	B	C	D
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	1